
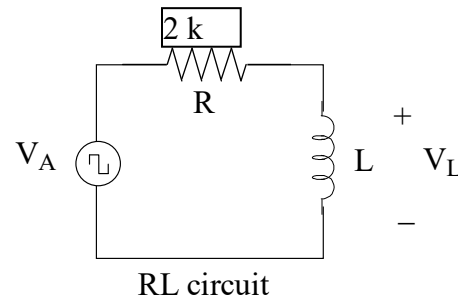


## LAB 8 - RC & RL STEP RESPONSE (2h)

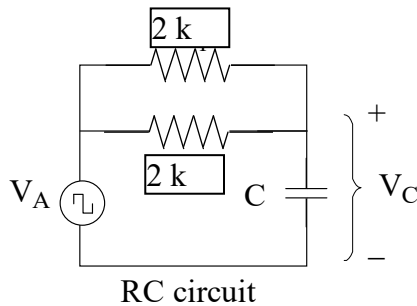

Step response is obtained by the sudden application - or removal - of a DC voltage. We will achieve this STEP INPUT by applying a square wave from the function generator. RC and RL circuits have a characteristic response to this input, and in this lab we will investigate this response.

### 8.1 EQUIPMENT LIST

1. Trainer
2. Oscilloscope (+ scope probes)
3. Function Generator (+ BNC cable, break-out cable, BNC-T splitter)
4. Resistors - 2 k $\Omega$  (x2)
5. Capacitor, 0.1  $\mu$ F
6. Inductor L (unknown value)
7. Potentiometer (~ 100 k $\Omega$ , to vary  $\tau$  continuously)
8. STUDENTS BRING A USB FLASH DRIVE
9. (\*\*\*) Measure component values with DMM
10. Note - if the scope trace seems to "jiggle", reset the scope (Save/Recall > Default Setup)


### 8.2 RC STEP RESPONSE

We will analyze the step response of an RC circuit. Theory tells us that an RC circuit will respond to a step as an exponential decay curve. The speed of the decay is quantified in a single value - the time constant. We will check the theoretical time constant against a measured one.

#### 8.2.1 Obtain a nice Display

##### STEPS

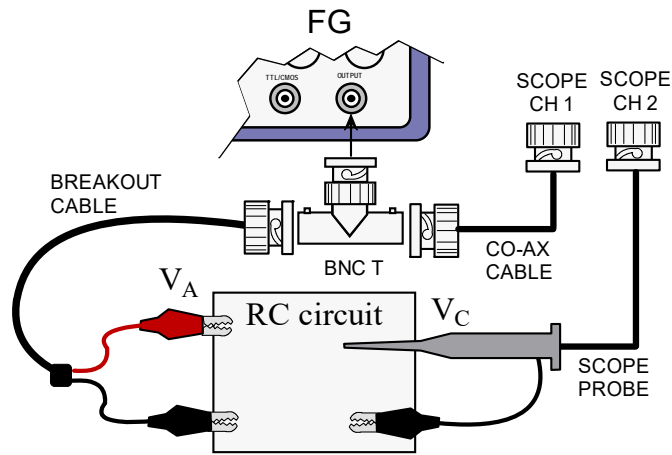1. Construct the RC circuit shown in figure above (power off).  $R = 2\text{ k}$ ,  $C = 0.1\text{ uF}$  (C closest to GND).
2. Note  $V_A$  means "applied voltage".  $V_C = V$  across C (capacitor).
3. Set  $V_A$  from FG (SQUARE wave, 3 V<sub>pp</sub>, ~ 560 Hz, 0 DC offset). (**check FG param's**)
4. Verify probe attenuation is correct (1x for co-ax cable, 10x for scope probe).
5. After completing the circuit, turn trainer ON.



Get both  $V_{in}$  (input) and  $V_c$  (output) to appear nicely on the scope.  
 Display both CH 1 & CH 2. Set both channels to DC coupling.  
 Overlay the traces using vertical positioning knobs. Set vertical position to 0 for BOTH channels.  
 Do NOT use Autoset which will offset them.  
 Adjust the voltage scale so the height of a full square wave can be seen  
 Adjust the time scale to get half of a period to show. Then adjust the horizontal (time) position so the trace wave looks something like the figure shown. Voltage scale should be same for both traces.


### 8.2.2 Measure RC Time Constant

Measure the time constant of the exponential curve using CURSORS function.

#### STEPS

1. Press "Cursor" key.
2. Set Source to CH 2 (press F1).
3. Press "Horizontal" or "Vertical" key to scroll through 4 choices for adjusting the cursors.
  - Choices: no cursors (2 dotted lines)
  - Adjust both cursors simultaneously (2 solid lines)
  - Adjust cursor 1 only (1 line solid, 1 line dotted... the solid line is the one that adjusts).
  - Adjust cursor 2 only (1 line dotted, the other line solid... The solid line adjusts).
4. Then adjust cursors by turning the "variable" knob.
5. Set cursors to the "start point" (see figure).
  - Set the bottom "vertical" (voltage) cursor to  $V_1$  level.
  - The start point can be anywhere on the response curve, but it is best here.
  - Note - vertical cursors appear as horizontal lines
6. Set the top "vertical" cursor to the  $V_2^*$  position
  - (at the square wave... where the response curve is "trying" to go).
  - This location is CRITICAL for accurate results.
7. Record the  $\Delta V$  value.
8. Multiply  $\Delta V$  by .632 and record.
9. Now move the top "vertical" cursor until you have the value you just recorded.
10. Turn on "Horizontal" cursors (button F2) to measure time values ( $T_1$  &  $T_2$ ).
  - Note - horizontal cursors are vertical lines
11. Adjust the left cursor to align with where  $V_1$  crosses the response curve (this is  $T_1$  in figure).
12. Adjust the right cursor to coincide with " $T_2$ " (where  $V_2$  crosses the response trace).
13. (\*\*\*) Record  $\Delta t$  (" $\Delta$ " in lower right of  $T_1$  &  $T_2$ ). This is  $\tau$  (actual) (in ms).

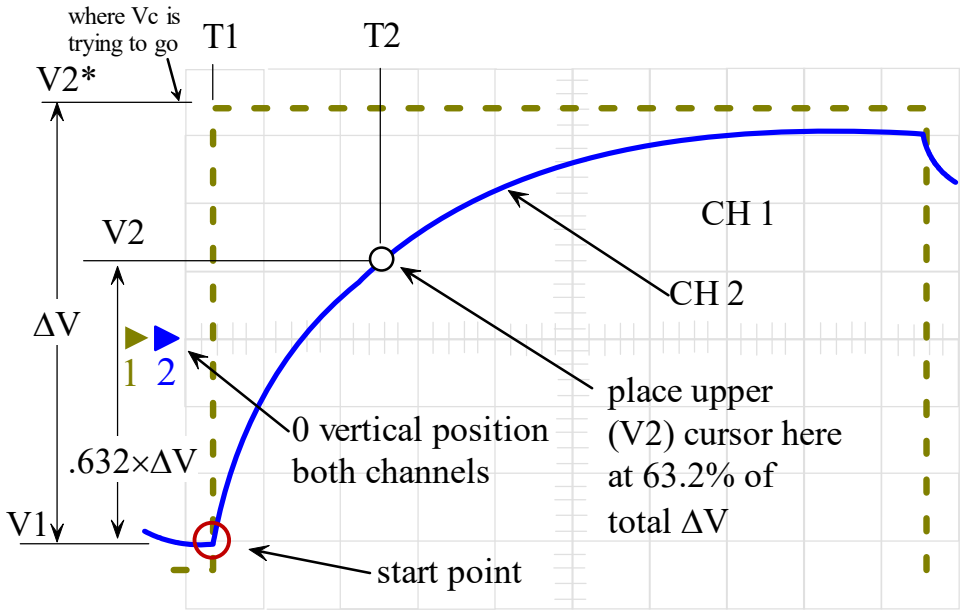- 14. (\*\*\*) Compute  $\tau$  (theory) using measured values of R and C (in ms).
- 15. (\*\*\*) Capture the trace (include voltage & cursors specifying tau.)




**8.2.3 Alter Time Constant**

Remove one of the resistors.  
 The response curve should change.

- (\*\*\*) Capture the trace (include voltage & cursors specifying tau.)

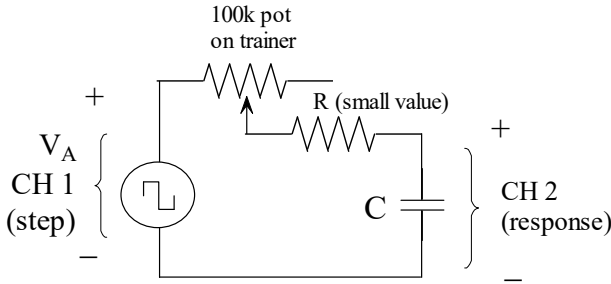**8.2.4 Continuous Change in Time Constant**



Here we will use a variable resistance (a potentiometer). Now we can continuously change the response curve.

**STEPS**

1. Build the circuit shown. ( $R = 2\text{ k}$ )
2. Turn the dial on the pot and observe the changes to the exponential response curve.


## 8.3 RL RESPONSE (TO COMPUTE L)

### 8.3.1 Measure RL Time Constant

Here we will measure the time constant of an RL circuit. The inductor L will have an unknown value, and we will use the time constant to estimate the value of L.

#### STEPS

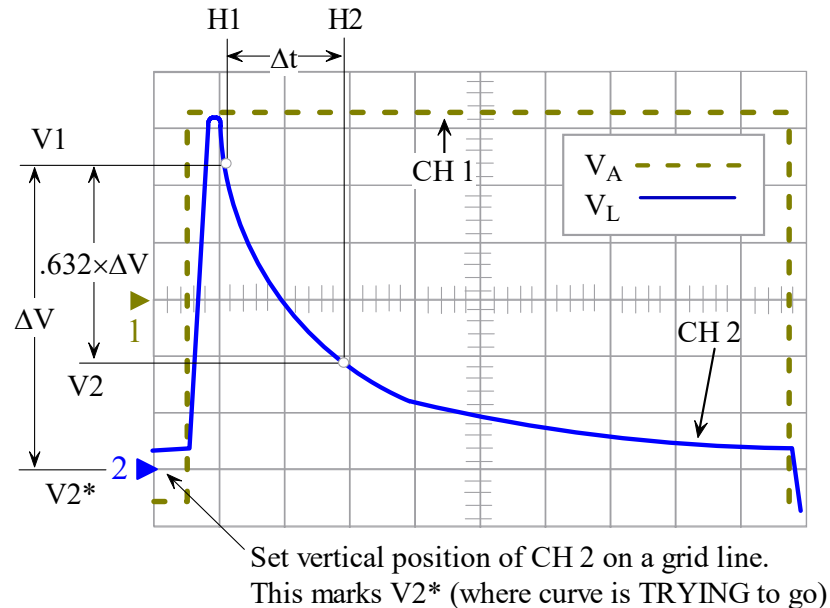1. Construct the RL circuit shown in figure above.  $R = 2 \text{ k}$ ,  $L = \text{unknown}$ . (L closer to GND).
2. Set  $V_A$  to be from FG (SQUARE wave,  $1 \text{ Vpp}$ ,  $\sim 60\text{-}70 \text{ kHz}$ ,  $0 \text{ DC offset}$ ). (**check FG params**)
3. Adjust the voltage and time scales to fill the display with the full square wave & HALF a period.
4. Overlay the 2 traces ( $0 \text{ V}$  vertical offset for both). Do NOT use Autoset.
5. Display both  $V_A$  (CH 1) and  $V_L$  (CH 2) on the scope.
6. Ensure probe attenuation is correct ( $1x$  for co-ax cable,  $10x$  for scope probe).
7. Adjust scope to fill screen with signals overlapped as shown below.
8. Adjust horizontal position so a full half period is shown.
9. Adjust the vertical position of both channels to  $0.0\text{V}$  (initially). Do not use Autoset.
10. Then alter the CH2 vertical position downward so its 'zero position' is aligns with a grid line. This will be the voltage level that the response curve is "trying to go to" ( $V2^*$ ). This point may not align with the kink in the trace!
11. Use CURSORS to measure the time constant on the response curve as before.
12. (\*\*\*) Record time constant



#### 16. Compute L

- a. (\*\*\*) Write the equation for  $\tau$  for RL circuits.
- b. (\*\*\*) Re-arrange equation to solve for L.
- b. (\*\*\*) Compute value of L using measured values of  $\tau$  and R (in mH)

# LAB 8 - ANSWER SHEET

## RC & RL STEP RESPONSE

Team Number: \_\_\_\_\_

Name 1: \_\_\_\_\_

Name 2: \_\_\_\_\_

8.1 Component Values

R (2 kΩ) \_\_\_\_\_

C (0.1 μF) \_\_\_\_\_


8.2 RC Step Response

$\tau$  (theory, ms) : \_\_\_\_\_.


$\tau$  (theory, ms): \_\_\_\_\_.

$\tau$  (measured, ms): \_\_\_\_\_.

$\tau$  (measured, ms): \_\_\_\_\_.

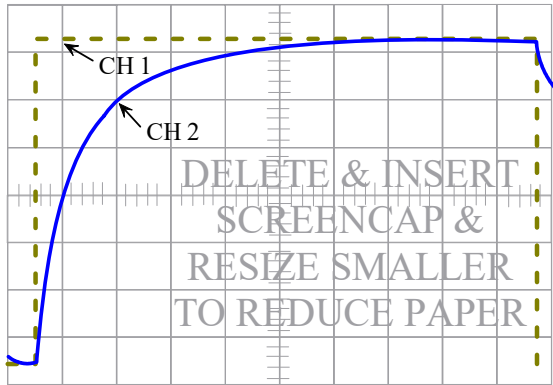

RC STEP RESPONSE

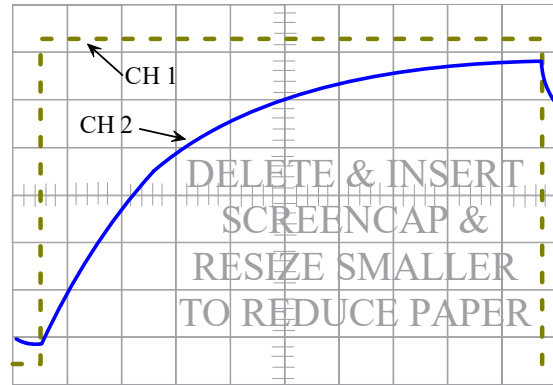

RC STEP RESPONSE with altered R


8.3 RL Step Response

\_\_\_\_\_  
 \_\_\_\_\_  
 \_\_\_\_\_  
 \_\_\_\_\_

$\tau$  (measured, μs)  
 $\tau$  equation for RL circuits  
 Re-arrange equation to solve L  
 Computed L value (in mH)

Show work below:

\_\_\_\_\_

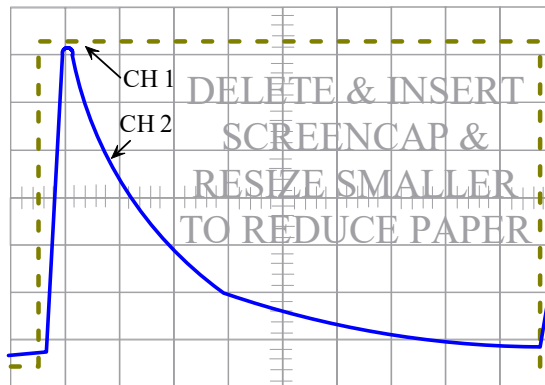

RL STEP RESPONSE